

# Chapter 11

## Capacitors

11.1 (a) see text, (b) yes

11.2 (a)  $4.05\ \Omega$ , (b)  $2.03\ \Omega$ , (c)  $7.4\ \text{A}$ , (d) infinity, (e) zero

11.3  $660\ \text{nC}$

11.4 (a)  $4.05\ \Omega$ , (b)  $3.9\ \mu\text{F}$ , (c)  $59\ \mu\text{C}$

11.5 (a)  $450\ \mu\text{J}$ , (b)  $450\ \mu\text{J}$ , (c)  $9.8\ \text{J}$ , (d) between the two

11.6  $9\ \Omega$

11.7 (a) No, (b) no, (c) yes, with the  $2.4\text{-}\mu\text{F}$  capacitor in series with the two  $2\text{-}\mu\text{F}$  capacitors in parallel

11.8 (a) yes, (b) the  $3\text{-}\mu\text{F}$  capacitor

11.9 The capacitance doubles

11.10  $6\ \mu\text{F}$

11.11 The maximum current through the circuit