

1. Two resistors, 42.0 and 64.0 Ohms, are connected in parallel to a voltage source. The current through the 64.0 Ohm resistor is 3.00 A. Determine the current in the other resistor.

- A) 1.97 A
- B) 3.00 A
- C) 4.57 A
- D) 7.57 A

$$(3 A) \frac{64}{42} = 4.57$$

2. If a 9 V battery supplies 4.5 A when its terminals are short-circuited, what is the internal resistance of the battery?

- A) 2  $\Omega$
- B) 0.5  $\Omega$
- C) 40.5  $\Omega$
- D) 18  $\Omega$


3. Chapter 20, Problem 68. A battery has an internal resistance of 0.012  $\Omega$  and an emf of 9.00 V. What is the maximum current that can be drawn from the battery without the terminal voltage dropping below 8.90 V? (Hint: Consider the internal resistance to be in series with an external resistance R. If  $V_R$  is 8.90 V, what is  $V_{0.012}$ ? What current would cause that  $V_{0.012}$ ?)

- A) 750 A
- B) 740 A
- C) 250 A
- D) 16 A
- E) 8.3 A

$$V_T = V_0 - IR_{int}$$

$$IR_{int} = V_0 - V_T = 0.1 V \quad I = \frac{0.1 V}{0.012 \Omega} = 8.3 A$$

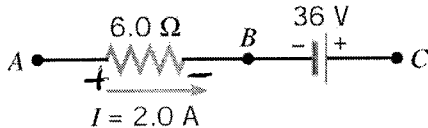A current of 2.0 A exists in the partial circuit shown in the drawing.



4. Chapter 20, Problem 74(a). What is the magnitude of the potential difference between the points A and B?

- A) 12 V
- B) 18 V
- C) 48 V
- D) 36 V
- E) 24 V

$$V = IR = (2.0 A)(6.0 \Omega) = 12 V$$

5. Chapter 20, Problem 74(b). What is the magnitude of the potential difference between points A and C?

- A) 12 V
- B) 18 V
- C) 48 V
- D) 36 V
- E) 24 V

$$\text{From } A \rightarrow B: 12 V \text{ drop} = -12 V$$

$$\text{From } B \rightarrow C: 36 V \text{ rise} = +36 V$$

$$\text{Total From } A \rightarrow C = +24 V$$

