

1. How many electrons flow through a battery that delivers a current of 3.0 A for 12 s?

- a) 4
- b) 36
- c) 4.8×10^{15}
- d) 6.4×10^{18}
- e) 2.2×10^{20}


$$Q = I \Delta t = (3.0 \text{ A})(12 \text{ s}) = 36 \text{ C}$$

$$N = \frac{Q}{e} = \frac{36 \text{ C}}{1.6 \times 10^{-19} \text{ C}} = 2.25 \times 10^{20} \text{ electrons}$$

2. The potential difference across the ends of a wire is doubled in magnitude. If Ohm's law is obeyed, which one of the following statements concerning the resistance of the wire is true?

- a) The resistance is one half of its original value.
- b) The resistance is twice its original value.
- c) The resistance is not changed.
- d) The resistance increases by a factor of four.
- e) The resistance decreases by a factor of four.

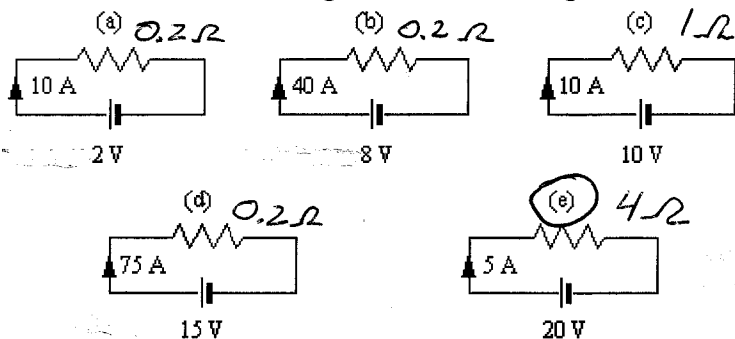3. Which one of the following circuits has the largest resistance?



4. When a light bulb is connected to a 4.5 V battery, a current of 0.16 A passes through the bulb filament. What is the resistance of the filament?

- a) 440 Ω
- b) 28 Ω
- c) 9.3 Ω
- d) 1.4 Ω
- e) 0.72 Ω

$$R = \frac{V}{I} = \frac{4.5 \text{ V}}{0.16 \text{ A}} = 28.1 \text{ } \Omega$$

5. Determine the length of a copper wire that has a resistance of 0.172 Ω and cross-sectional area of $1 \times 10^{-4} \text{ m}^2$. The resistivity of copper is $1.72 \times 10^{-8} \text{ } \Omega \cdot \text{m}$.

- a) 0.1 m
- b) 10 m
- c) 100 m
- d) 1000 m
- e) 10 000 m

$$R = \frac{\rho L}{A} \rightarrow L = \frac{RA}{\rho} = \frac{(0.172 \text{ } \Omega)(1 \times 10^{-4} \text{ m}^2)}{1.72 \times 10^{-8} \text{ } \Omega \cdot \text{m}} = 1000 \text{ m}$$

6. Complete the following statement: The unit *kilowatt • hour* measures

- a) current.
- b) energy.
- c) power.
- d) potential drop.
- e) voltage.

It is energy as sold by the power company.

7. A 40-W and a 60-W light bulb are designed for use with the same voltage. What is the ratio of the resistance of the 60-W bulb to the resistance of the 40-W bulb?

- a) 1.5
- b) 0.67
- c) 2.3
- d) 0.44
- e) 3.0

$$P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P} \rightarrow \frac{R_{60}}{R_{40}} = \frac{40}{60} = 0.67$$

8. A computer monitor uses 2.0 A of current when it is plugged into a 120 V outlet. The monitor is never turned off. What is the yearly cost of operating the monitor if the cost of electricity is \$0.12/kWh?

- a) \$14
- b) \$21
- c) \$98
- d) \$170
- e) \$250

$$P = IV = (2.0 \text{ A})(120 \text{ V}) = 240 \text{ W}$$

$$\text{Energy} = P \Delta t = (240 \text{ W})(1 \text{ year}) \left(\frac{1 \text{ kW}}{1000 \text{ W}} \right) \left(\frac{8766 \text{ hr}}{1 \text{ year}} \right) = 2104 \text{ kWh}$$

9. A 4-A current is maintained in a simple circuit with a total resistance of 2 Ω . How much energy is dissipated in 3 seconds?

- a) 3 J
- b) 6 J
- c) 12 J
- d) 24 J
- e) 96 J

$$P = I^2 R = (4 \text{ A})^2 (2 \Omega) = 32 \text{ W}$$

$$\text{Energy} = P \Delta t = (32 \text{ W})(3 \text{ s}) = 96 \text{ J}$$

10. Which one of the following statements concerning resistors **in series** is true?

- a) The voltage across each resistor is the same.
- b) The current through each resistor is the same.
- c) The power dissipated by each resistor is the same.
- d) The rate at which charge flows through each resistor depends on its resistance.
- e) The total current through the resistors is the sum of the current through each resistor.

11. Three resistors, 50- Ω , 100- Ω , 200- Ω , are connected in series in a circuit. What is the equivalent resistance of this combination of resistors?

- a) 350 Ω
- b) 250 Ω
- c) 200 Ω
- d) 120 Ω
- e) 29 Ω

$$R_T = R_1 + R_2 + R_3 \\ = 50 \Omega + 100 \Omega + 200 \Omega = 350 \Omega$$

12. Two 15-Ω and three 25-Ω light bulbs and a 24 V battery are connected in a series circuit. What is the current that passes through each bulb?

- a) 0.23 A
- b) 0.51 A
- c) 0.96 A
- d) 1.6 A
- e) The current will be 1.6 A in the 15-Ω bulbs and 0.96 A in the 25-Ω bulbs.

$$R_T = 15\Omega + 15\Omega + 25\Omega + 25\Omega + 25\Omega = 105\Omega$$

$$I = V/R = 24V / 105\Omega = 0.229 A$$

13. Three resistors, 6.0-Ω, 9.0-Ω, 15-Ω, are connected in parallel in a circuit. What is the equivalent resistance of this combination of resistors?

- a) 30 Ω
- b) 10 Ω
- c) 3.8 Ω
- d) 2.9 Ω
- e) 0.34 Ω

$$\frac{1}{R_p} = \frac{1}{6\Omega} + \frac{1}{9\Omega} + \frac{1}{15\Omega} = 0.344 \rightarrow R_p = 2.9\Omega$$

14. A non-ideal battery has a 6.0-V *emf* and an internal resistance of 0.6 Ω. Determine the terminal voltage when the current drawn from the battery is 1.0 A.


- a) 5.0 V
- b) 6.0 V
- c) 5.4 V
- d) 6.6 V
- e) 5.8 V

$$V_{\text{terminal}} = V_0 - IR_{\text{int}} = (6.0V) - (1.0A)(0.6\Omega)$$

$$= 5.4V$$

Use the following to answer questions 15-16:

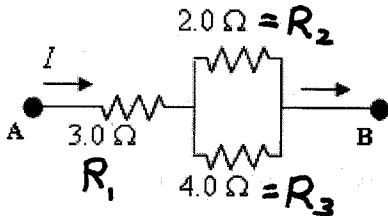Three resistors are connected as shown in the figure. The potential difference between points A and B is 26 V.



	R	I	V
R ₁	3Ω	③ 6 A	④ 18 V
R ₂	2Ω	② 4 A	⑤ 8 V
R ₃	4Ω	⑦ 2 A	⑤ 8 V
Tot	① 4.33Ω	② 6 A	26V

15. What is the equivalent resistance between the points A and B?

- a) 3.8 Ω
- b) 4.3 Ω
- c) 5.1 Ω
- d) 6.8 Ω
- e) 9.0 Ω

$$R_T = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = 4.33\Omega$$

Series
Parallel

16. How much current flows through the 2-Ω resistor?

- a) 2.0 A
- b) 4.0 A
- c) 6.0 A
- d) 8.7 A
- e) 10.0 A

① $R_{T\text{tot}} = 4.33\Omega$

② $I_{\text{Tot}} = \frac{26V}{4.33\Omega} = 6A$

③ $I_1 = I_{\text{Tot}} = 6A$

④ $V_1 = I_1 R_1 = (6A)(3\Omega) = 18V$

⑤ $V_{23} = V_T - V_1 = 26V - 18V = 8V$

⑥ $I_2 = V_2 / R_2 = 8V / 2\Omega = 4A$